

Tutorial 7

Problems of Combinational Logic

Exercise 1 Polling Report

Four shop stewards (A , B , C , D) represent the following number of votes respectively: 100 votes, 150 votes, 250 votes and 175 votes. A proposal needs at least 50 % of the votes to be accepted. Write down the most simplified expression of a logic function (S) that is 1 when a proposal is accepted and 0 when it is rejected. Draw the circuit diagram.

Indication: ' $A = 1$ ' means that the A shop steward accepts a proposal and ' $A = 0$ ' means that he or she rejects it. The same goes for the other shop stewards.

Exercise 2 Liquid Level

Let us consider two tanks: $R1$ and $R2$. The liquid level of each tank is checked by two sensors: a high-level sensor (A for $R1$, B for $R2$) and a low-level sensor (C for $R1$, D for $R2$). The values of A , B , C , D are 1s when there is some liquid in front of the sensor; otherwise they are 0s. Three indicator lights ($V1$, $V2$, $V3$) are set according to the following conditions:

- $V1 = 1$, if $R1$ and $R2$ are full.
- $V2 = 1$, if $R1$ and $R2$ are empty.
- $V3 = 1$, in any other cases.

Write down the truth tables and the most simplified expressions of the outputs. Draw the circuit diagram.