

Tutorial 6

Karnaugh Maps

Exercise 1

Let us consider N , a number encoded in 3 bits (C, B, A). A is the least significant bit. Using Karnaugh maps, write down the most simplified expression of $S = f(N)$ for each of the following:

- $S = 1$ when $N \geq 3$
- $S = 1$ when $2 < N \leq 6$
- $S = 1$ when $N = 1, 3$ or 5
- $S = 1$ when $N = 1, 3$ or 5 and S is undefined when $N = 0$ or 4

Exercise 2

We want to design a circuit that performs the two's complement operation. This circuit has three inputs (C, B, A) and three outputs (C', B', A'). A and A' are the least significant bits.

1. Write down the truth table for the three outputs.
2. Write down their most simplified expressions.

We want to design a circuit that converts a natural binary number into a Gray code number. This circuit has three inputs (C, B, A) and three outputs (C', B', A'). A and A' are the least significant bits.

3. Write down the truth table for the three outputs.
4. Write down their most simplified expressions.

Exercise 3

Let us consider N , a number encoded in 4 bits (D, C, B, A). A is the least significant bit. Using Karnaugh maps, write down the most simplified expression of $S = f(N)$ for each of the following:

- $S = 1$ when $N \geq 10$
- $S = 1$ when $N = 0, 4, 8, 10, 12$ or 14
- $S = 1$ when $N = 0, 2, 5, 7, 8, 10, 13$ or 15
- $S = 1$ when $N = 2, 10, 11$ or 14
- $S = 1$ when $N = 2, 10, 11$ or 14 and S is undefined when $N = 6, 9, 13$ or 15