

Key to Tutorial 5

Memory Devices

Exercise 1

Let us consider the two following ROM devices:



1. How many 4-bit words does the memory device **M1** contain?

We have to work out the depth of the memory device **M1**.

$256 \text{ Kib} = (256 \text{ Ki} / 4) \text{ words of 4 bits} = 64 \text{ Ki words of 4 bits.}$

The memory device M1 contains 64 Ki words of 4 bits.

2. How many 8-bit words does the memory device **M2** contain?

We have to work out the depth of the memory device **M2**.

$512 \text{ Kib} = (512 \text{ Ki} / 8) \text{ words of 8 bits} = 64 \text{ Ki words of 8 bits.}$

The memory device M2 contains 64 Ki words of 8 bits (64 KiB).

3. How many address lines does each of the two memory devices have?

The number of address lines can be determined from the memory depth.

$64 \text{ Ki words} = 2^{16} \text{ words.}$

Both of the memory devices have 16 address lines.


A memory device **M2** should be built from two memory devices **M1**.

4. In which way should the memory devices be connected to each other?

A 4-bit data bus must be turned into an 8-bit data bus.

Therefore, 2 memory devices M1 should be connected in parallel.

5. Draw the circuit diagram.

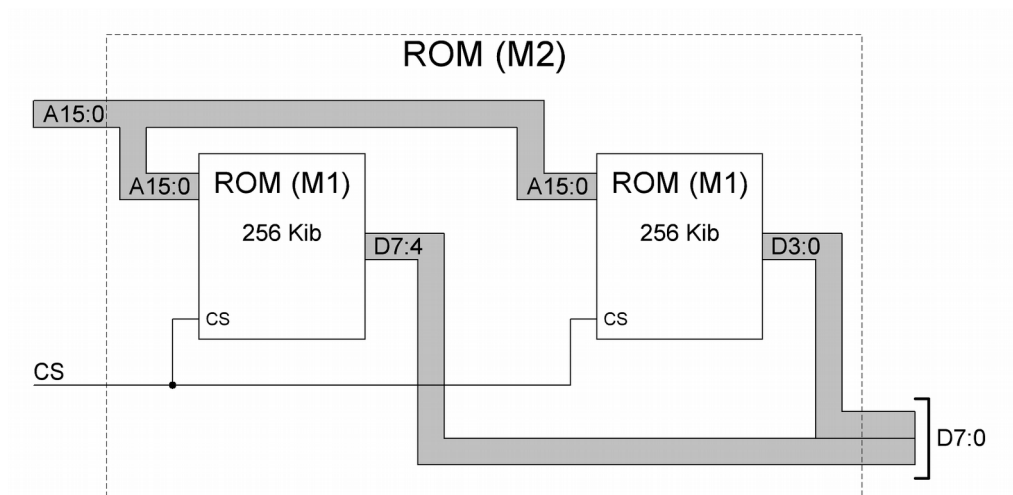

Exercise 2

A RAM device (**M1**) has a capacity of 2 Mib, a 4-bit data bus, a *CS* input and a *WE* input. A RAM device (**M2**) has a capacity of 4 Mib. The data and control buses of these two RAM devices are identical. A memory device **M2** should be built from several memory devices **M1**.

1. Work out the number of address lines for each of the two memory devices.

The number of address lines can be determined from the memory depth.

M1: 2 Mib = (2 Mi / 4) words of 4 bits = 512 Ki words of 4 bits.

512 Ki words = 2^{19} words.

The memory device M1 has 19 address lines.

M2: 4 Mib = (4 Mi / 4) words of 4 bits = 1 Mi words of 4 bits.

1 Mi words = 2^{20} words.

The memory device M2 has 20 address lines.

2. In which way should the memory devices be connected to each other?

A 19-bit address bus must be turned into a 20-bit address bus.

Therefore, 2 memory devices M1 should be connected in series.

3. How many address lines are required to control the *CS* input of each memory device **M1**?

The memory device **M2** has one more address line than the memory device **M1** ($20 - 19 = 1$).

This address line should be used to control the *CS* of each memory device M1.


4. Draw the circuit diagram.

Each *WE* input of the memory devices **M1** is connected to the *WE* inputs of the memory device **M2**. There is no particular difficulty for these kinds of entries.

A demultiplexer should be used to select one of the memory devices **M1**. This demultiplexer will be controlled by the address line *A19*.

- When $A19 = 0$, the *CS* of the memory device **M2** is transferred to the *CS* of the first memory device **M1** (at the top of the diagram). The other output of the demultiplexer is set to 0 and the second memory device **M1** (at the bottom of the diagram) is deactivated.
- When $A19 = 1$, the *CS* of the memory device **M2** is transferred to the *CS* of the second memory device **M1**. The other output of the demultiplexer is set to 0 and the first memory device **M1** is deactivated.

It can be noticed that when $CS = 0$, both of the memory devices **M1** are deactivated.

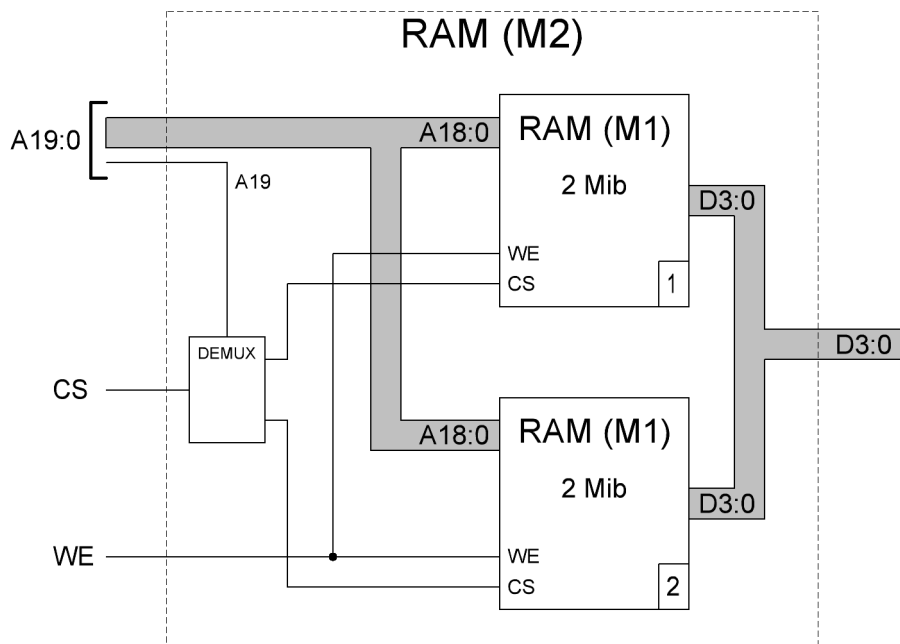5. Which memory device **M1** is selected when the address 515_{10} is being read?

The address line *A19* controls the demultiplexer; in other words, *A19* selects the first or the second memory device **M1**.

$515_{10} = 00203_{16} \rightarrow A19 = 0 \rightarrow$ **The memory device M1 number 1 is selected.**

6. Which memory device **M1** is selected when the address $9A844_{16}$ is being written?

Using the same line of reasoning:

$9A844_{16} \rightarrow A19 = 1 \rightarrow$ **The memory device M1 number 2 is selected.**

Exercise 3

A RAM device (**M1**) has a capacity of 512 bytes and a 4-bit data bus. A RAM device (**M2**) has a capacity of 8 KiB and a 16-bit data bus. A memory device **M2** should be built from several memory devices **M1**.

1. Work out the number of cells and the size of the address bus for the two memory devices.

M1 : 512 bytes = $(512 \times 8 / 4)$ words of 4 bits = **1 Ki words of 4 bits**.

1 Ki words = 2^{10} words.

The memory device M1 has 10 address lines and 1 Ki cells.

M2 : 8 KiB = $(8 \text{ Ki} \times 8 / 16)$ words of 16 bits = **4 Ki words of 16 bits**.

4 Ki words = 2^{12} words.

The memory device M2 has 12 address lines and 4 Ki cells.

2. How many memory devices should be put in series?

A depth of 1 Ki words must be turned into a depth of 4 Ki words.

Therefore, 4 memory devices should be put in series ($4 \text{ Ki} / 1 \text{ Ki} = 4$).

3. How many memory devices should be put in parallel?

A 4-bit data bus must be turned into a 16-bit data bus.


Therefore, 4 memory devices should be put in parallel ($16 / 4 = 4$).

4. How many address lines are required to control the CS input of each memory device **M1**?

The memory device **M2** has two more address lines than the memory device **M1** ($12 - 10 = 2$).

These two address lines should be used to control the CS of each memory device M1.

5. Draw the circuit diagram.

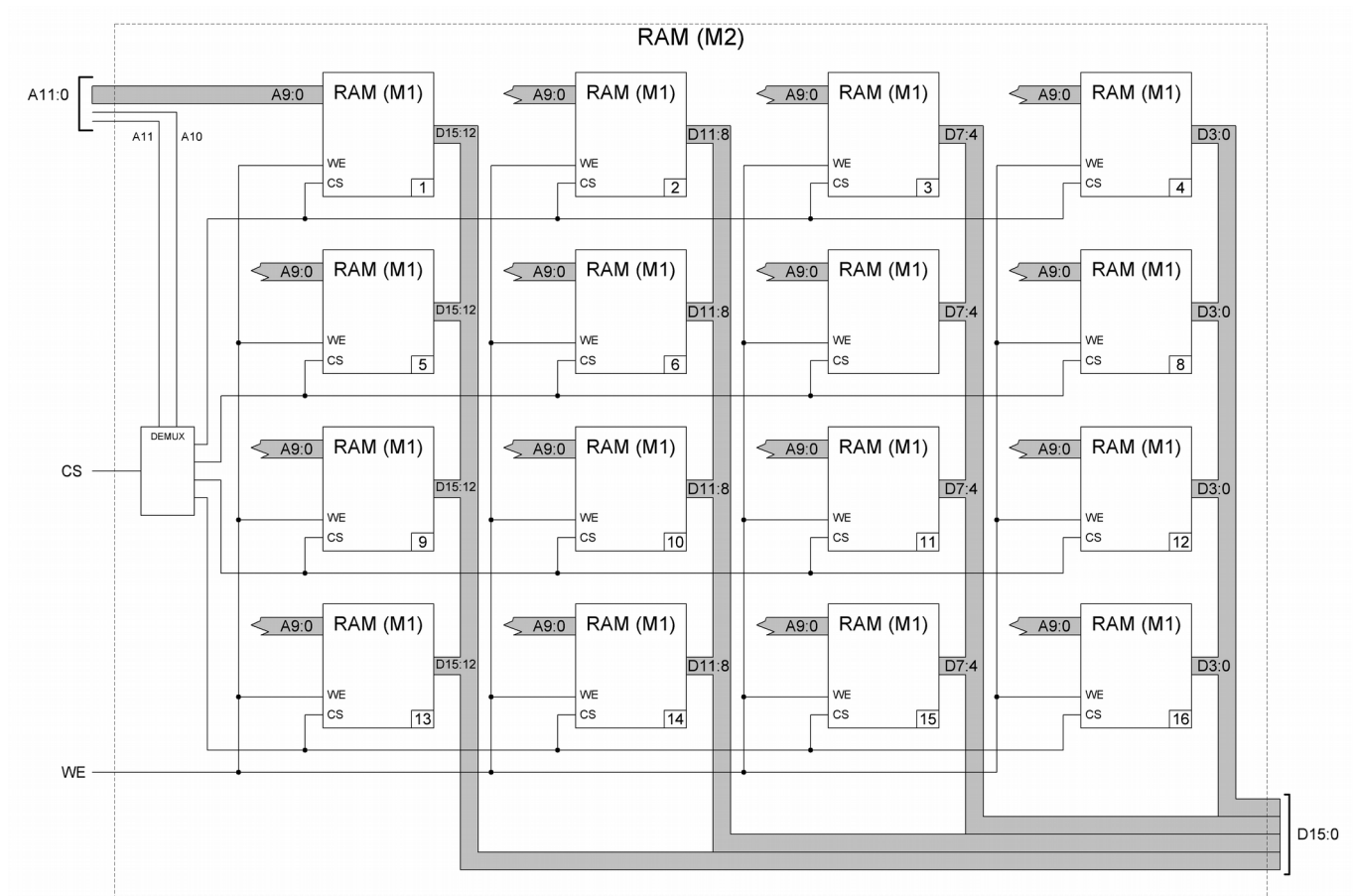
6. Which memory devices **M1** are selected for each of the following addresses: $95A_{16}$, $E03_{16}$, $1FF_{16}$, 725_{16} .

For each address, we have to find the values of $A11$ and $A10$.

- $95A_{16}$: $A11 = 1$, $A10 = 0$: the memory devices **M1** number 9, 10, 11 and 12 are selected.
- $E03_{16}$: $A11 = 1$, $A10 = 1$: the memory devices **M1** number 13, 14, 15 and 16 are selected
- $1FF_{16}$: $A11 = 0$, $A10 = 0$: the memory devices **M1** number 1, 2, 3 and 4 are selected.
- 725_{16} : $A11 = 0$, $A10 = 1$: the memory devices **M1** number 5, 6, 7 and 8 are selected.

Exercise 4

The memory device below has a few mistakes. Find them and correct them.

 **Indications :**

- The number of memory devices **M1** is right.
- The capacity (in bits) of the memory device **M1** is right.
- The size of the data bus of the memory device **M1** is right.
- Parallel connections are displayed horizontally.
- Series connections are displayed vertically.

From the indications above, we can work out the number of address lines for each memory device:

M1: 1 Kib = (1 Ki / 4) words of 4 bits = 256 words of 4 bits = 2^8 words of 4 bits.

The memory device **M1** has 8 address lines ($A7:0$).

M2: Since two blocks of **M1** are connected in series, **M2** has one more address line than **M1**.

The memory device **M2** has 9 address lines ($A8:0$).

Since two blocks of **M1** are connected in parallel, the data bus of **M2** is twice as wide as the data bus of **M1**. Therefore, the memory device **M2** has an 8-bit data bus ($D7:0$).

There is never an input \overline{WE} (Write Enable) on a ROM device (Read Only Memory).

A demultiplexer should be used to handle the inputs CS .

We obtain the following circuit diagram:

