

# Tutorial 8

## Arithmetical Operations

### Exercise 1: BCD Multiplication

Let us consider  $N$ , a 4-bit unsigned number:  $N = DCBA$  ( $A$  is the least significant bit) and  $N < 10$ . We want to design a circuit that multiplies  $N$  by 2. The result should be encoded in a BCD form and so be made up of 2 digits:  $H'G'F'E'$  for the tens column and  $D'C'B'A'$  for the units column ( $E'$  and  $A'$  are the least significant bits).

Write down the truth tables and the most simplified expressions of the outputs.

### Exercise 2: The Full Adder

Adding binary numbers (or numbers from any other bases) is very similar to adding decimal numbers. We add the digits of the same column to a possible carry from the previous column. We obtain a result and a possible carry that may be added to the next column.

A full adder is a circuit that adds two bits ( $A_i + B_i$ ) and a possible carry ( $R_{i-1}$ ). It generates the sum ( $S_i$ ) and a possible carry ( $R_i$ ).

We want to design a full adder.

1. Write down the truth tables of  $S_i$  and  $R_i$ .
2. Write down the Karnaugh maps and the most simplified expressions of  $S_i$  and  $R_i$ .
3. Draw the circuit diagram of the full adder.

Using four full adders, we want to design a 4-bit adder that performs a 4-bit addition of two numbers.

4. Draw the circuit diagram of the 4-bit adder.

### Exercise 3: The Full Subtractor

A full subtractor is a circuit that subtracts two bits ( $A_i - B_i$ ) and a possible borrow ( $R_{i-1}$ ). It generates the difference ( $D_i$ ) and a possible borrow ( $R_i$ ).

We want to design a full subtractor.

1. Write down the truth tables of  $D_i$  and  $R_i$ .
2. Write down the Karnaugh maps and the most simplified expressions of  $D_i$  and  $R_i$ .
3. Draw the circuit diagram of the full subtractor.

Using four full subtractors, we want to design a 4-bit subtractor that performs a 4-bit subtraction of two numbers.

4. Draw the circuit diagram of the 4-bit subtractor.

### **Exercise 4: Adder–Subtractor**

1. Design a circuit with one output ( $S$ ) that inverts or not an input ( $E$ ) according to the value of a control bit ( $C$ ):
  - If  $C = 0$ ,  $S = E$
  - If  $C = 1$ ,  $S = \overline{E}$
  
2. Using the circuit above and a 4-bit adder (designed in a previous exercise), build an adder–subtractor that adds or subtracts two 4-bit numbers. This circuit has two 4-bit inputs ( $A$ ,  $B$ ), a control input ( $C$ ), and a 4-bit output ( $S$ ):
  - If  $C = 0$ ,  $S = A + B$
  - If  $C = 1$ ,  $S = A - B$