

Key to Tutorial 6

Karnaugh Maps

Exercise 1

Let us consider N , a number encoded in 3 bits (C, B, A). A is the least significant bit. Using Karnaugh maps, write down the most simplified expression of $S = f(N)$ for each of the following:

- $S = 1$ when $N \geq 3$

		BA			
C	S	00	01	11	10
	0	0	0	1	0
	1	1	1	1	1

$$S = C + B.A$$

- $S = 1$ when $2 < N \leq 6$

		BA			
C	S	00	01	11	10
	0	0	0	1	0
	1	1	1	0	1

$$S = C.\bar{B} + C.\bar{A} + \bar{C}.B.A$$

$$S = C.(\bar{B} + \bar{A}) + \bar{C}.B.A$$

$$S = C.(B.\bar{A}) + \bar{C}.B.A$$

$$S = C \oplus (B.A)$$

- $S = 1$ when $N = 1, 3$ or 5

		BA			
C	S	00	01	11	10
	0	0	1	1	0
	1	0	1	0	0

$$S = \bar{B}.A + \bar{C}.A$$

- $S = 1$ when $N = 1, 3$ or 5 and S is undefined when $N = 0$ or 4

		BA			
C	S	00	01	11	10
	0	Φ	1	1	0
	1	Φ	1	0	0

$$S = \bar{B} + \bar{C}.A$$

Exercise 2

We want to design a circuit that performs the two's complement operation. This circuit has three inputs (C, B, A) and three outputs (C', B', A'). A and A' are the least significant bits.

1. Write down the truth table for the three outputs.

C	B	A	C'	B'	A'
0	0	0	0	0	0
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	0	0	1

2. Write down their most simplified expressions.

$A' = A$ (obvious solution)

		BA				
		B'	00	01	11	10
C	0	0	1	0	1	
	1	0	1	0	1	

$$B' = \overline{B}.A + B.\overline{A}$$

$$B' = B \oplus A$$

		BA				
		C'	00	01	11	10
C	0	0	1	1	1	
	1	1	0	0	0	

$$C' = \overline{C}.B + \overline{C}.A + C.\overline{B}.\overline{A}$$

$$C' = \overline{C}.(B + A) + C.\overline{B}.\overline{A}$$

$$C' = \overline{C}.(B + A) + C.(\overline{B+A})$$

$$C' = C \oplus (B + A)$$

We want to design a circuit that converts a natural binary number into a Gray code number. This circuit has three inputs (C, B, A) and three outputs (C', B', A'). A and A' are the least significant bits.

3. Write down the truth table for the three outputs.

C	B	A	C'	B'	A'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

4. Write down their most simplified expressions.

		BA				
		A'	00	01	11	10
C	0	0	1	0	1	
	1	0	1	0	1	

$$A' = \overline{B}.A + B.\overline{A}$$

$$A' = B \oplus A$$

		BA				
		B'	00	01	11	10
C	0	0	0	1	1	
	1	1	1	0	0	

$$B' = C.\overline{B} + \overline{C}.B$$

$$B' = C \oplus B$$

$C' = C$ (obvious solution)

Exercise 3

Let us consider N , a number encoded in 4 bits (D, C, B, A). A is the least significant bit. Using Karnaugh maps, write down the most simplified expression of $S = f(N)$ for each of the following:

- $S = 1$ when $N \geq 10$

		BA			
DC	S	00	01	11	10
	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	1

$S = D.C + D.B$

- $S = 1$ when $N = 0, 4, 8, 10, 12$ or 14

		BA			
DC	S	00	01	11	10
	00	1	0	0	0
	01	1	0	0	0
	11	1	0	0	1
	10	1	0	0	1

$S = D.\bar{A} + \bar{B}.\bar{A}$

- $S = 1$ when $N = 0, 2, 5, 7, 8, 10, 13$ or 15

		BA			
DC	S	00	01	11	10
	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1

$S = C.A + \bar{C}.\bar{A}$
 $S = C \oplus A$

- $S = 1$ when $N = 2, 10, 11$ or 14

		BA			
DC	S	00	01	11	10
	00	0	0	0	1
	01	0	0	0	0
	11	0	0	0	1
	10	0	0	1	1

$S = D.\bar{C}.B + D.B.\bar{A} + \bar{C}.B.\bar{A}$

- $S = 1$ when $N = 2, 10, 11$ or 14 and S is undefined when $N = 6, 9, 13$ or 15

There are two equivalent possibilities:

		BA				
		S	00	01	11	10
DC	00	0	0	0	0	1
	01	0	0	0	0	Φ
	11	0	Φ	Φ	Φ	1
	10	0	Φ	1	1	1

$$S = D.B + B.\overline{A}$$

or

		BA				
		S	00	01	11	10
DC	00	0	0	0	0	1
	01	0	0	0	0	Φ
	11	0	Φ	Φ	1	1
	10	0	Φ	1	1	1

$$S = D.A + B.\overline{A}$$