

Key to Final Exam S2

Computer Architecture

Duration: 1 hr 30 min.

Answer on the answer sheet only.

Do not show any calculation unless you are explicitly asked.

Do not use red ink.

Exercise 1 (5 points)

1. Convert the numbers given on the [answer sheet](#) into their **single-precision** IEEE-754 representations. Write down the final result in its **binary form** and specify the three fields.
2. Convert the **double-precision** IEEE-754 words given on the [answer sheet](#) into their associated representations. If a representation is a number, use the following base-10 form: $k \times 2^n$ where k and n are integers (either positive or negative).

Exercise 2 (4 points)

We want to build a 2-Mib ROM device (labelled M) from several 16-Kib ROM devices (labelled m). The M device has a 16-bit data bus. The m devices have a 4-bit data bus. Answer the questions on the [answer sheet](#).

Exercise 3 (5 points)

1. Wire the flip-flops ([figure 1](#)) in order to design a **modulo-11 asynchronous up counter**.
2. Wire the flip-flops ([figure 2](#)) in order to design a **modulo-11 asynchronous down counter**.
3. Wire the flip-flops ([figure 3](#)) in order to design a **shift register** ($E \rightarrow Q0 \rightarrow Q1 \rightarrow Q2 \rightarrow Q3$).

Exercise 4 (6 points)

The table shown on the [answer sheet](#) gives the sequence of a counter we want to design. This counter should be made up of JK flip-flops.

1. Complete the table shown on the [answer sheet](#).
2. Write down the most simplified expressions of J and K for each flip-flop on the [answer sheet](#). **Complete the Karnaugh maps for the solutions that are not obvious**. An obvious solution does not have any logical operations apart from the complement (for instance: $J0 = 1$, $K1 = \overline{Q2}$).

Last name: First name: Group:

ANSWER SHEET**Exercise 1**

1.

| Number | S | E | M |
|---------|---|----------|--------------------------|
| 75.75 | 0 | 10000101 | 001011110000000000000000 |
| 0.46875 | 0 | 01111101 | 111000000000000000000000 |

2.

| IEEE-754 Representation | Associated Representation |
|-----------------------------------|---------------------------|
| 20A1 8000 0000 0000 ₁₆ | 35×2^{-506} |
| 7FF7 0000 0000 0000 ₁₆ | NaN |
| 0004 2000 0000 0000 ₁₆ | $33 \times 2^{-1,029}$ |

Exercise 2

| Question | Answer |
|---|----------------------------------|
| What is the depth of the <i>m</i> memory? | 2¹² words |
| What is the depth of the <i>M</i> memory? | 2¹⁷ words |
| What is the number of address lines of the <i>m</i> memory? | 12 lines |
| What is the number of address lines of the <i>M</i> memory? | 17 lines |
| How many memory devices should be put in parallel? | 4 memory devices |
| How many memory devices should be put in series? | 32 memory devices |
| How many address lines are required to control the CS input of the memory devices? | 5 address lines |
| When the <i>M</i> memory is active, how many <i>m</i> memory devices are active simultaneously? | 4 <i>m</i> memory devices |

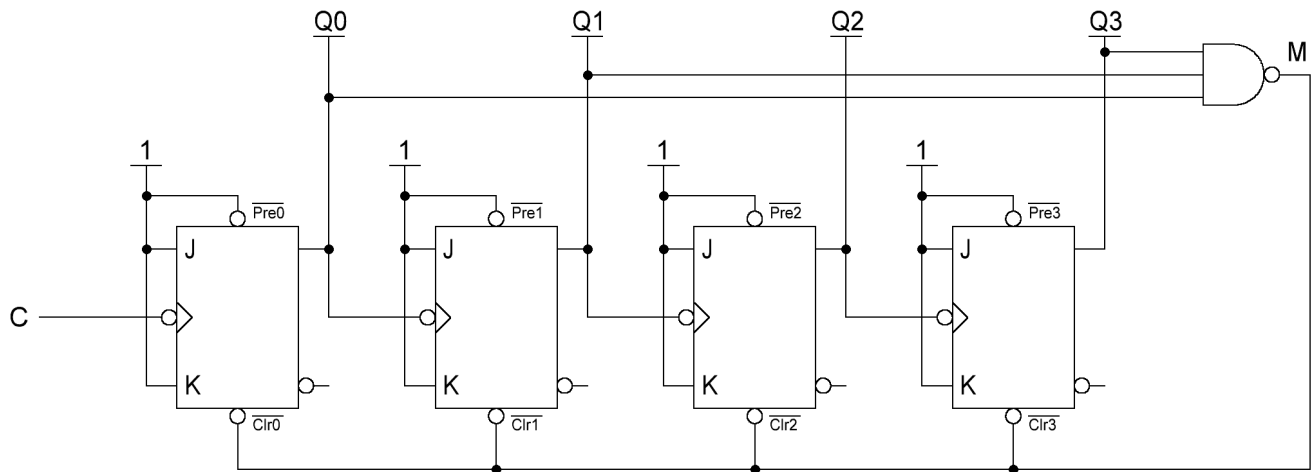
Exercise 3

Figure 1

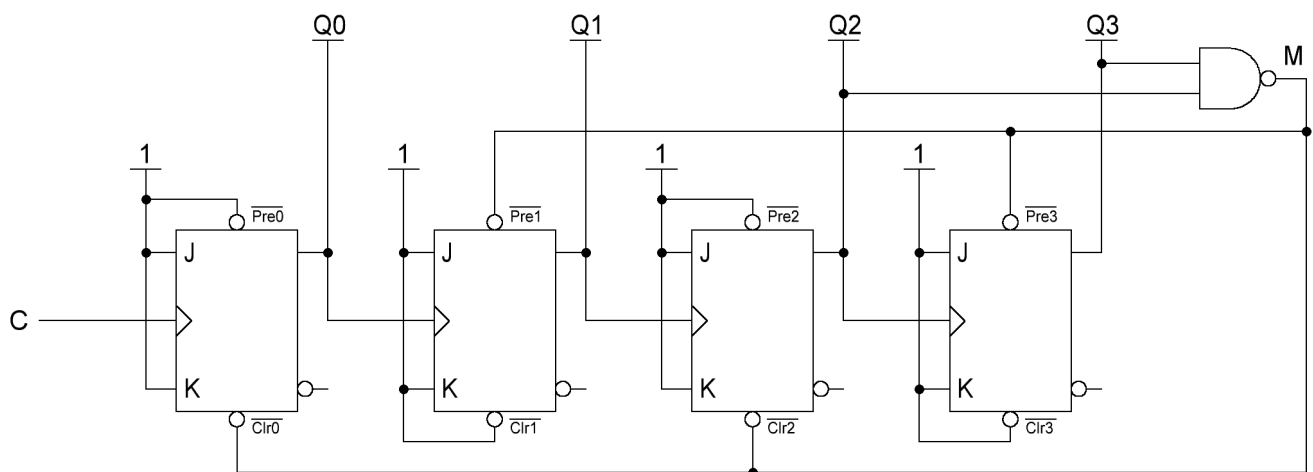


Figure 2

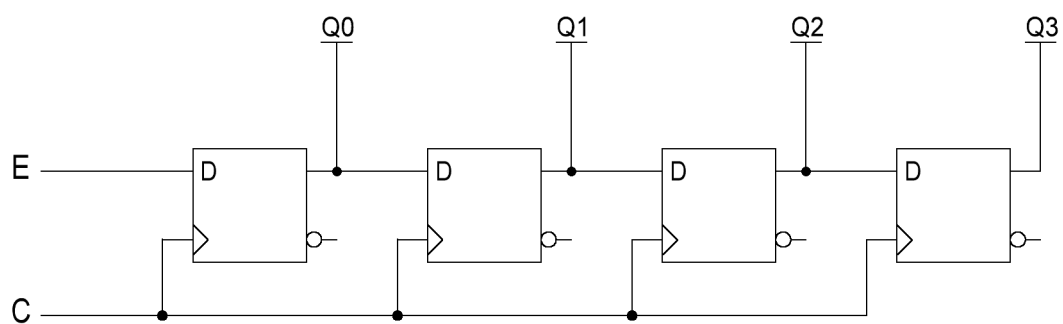


Figure 3

Exercise 4

| Q2 | Q1 | Q0 | J2 | K2 | J1 | K1 | J0 | K0 |
|----|----|----|--------|--------|--------|--------|--------|--------|
| 0 | 0 | 0 | 0 | Φ | 0 | Φ | 1 | Φ |
| 0 | 0 | 1 | 0 | Φ | 1 | Φ | Φ | 0 |
| 0 | 1 | 1 | 0 | Φ | Φ | 0 | Φ | 1 |
| 0 | 1 | 0 | 1 | Φ | Φ | 0 | 0 | Φ |
| 1 | 1 | 0 | Φ | 0 | Φ | 0 | 1 | Φ |
| 1 | 1 | 1 | Φ | 0 | Φ | 1 | Φ | 0 |
| 1 | 0 | 1 | Φ | 0 | 0 | Φ | Φ | 1 |
| 1 | 0 | 0 | Φ | 1 | 0 | Φ | 0 | Φ |

Do not use Karnaugh maps for obvious solutions.

Q1 Q0

| J0 | 00 | 01 | 11 | 10 |
|----|----|--------|--------|----|
| 0 | 1 | Φ | Φ | 0 |
| 1 | 0 | Φ | Φ | 1 |

$$J0 = \overline{Q1}.Q2 + Q1.Q2 = \overline{Q1} \oplus Q2$$

Q1 Q0

| K0 | 00 | 01 | 11 | 10 |
|----|--------|----|----|--------|
| 0 | Φ | 0 | 1 | Φ |
| 1 | Φ | 1 | 0 | Φ |

$$K0 = \overline{Q1}.Q2 + Q1.Q2 = Q1 \oplus Q2$$

Q1 Q0

| J1 | 00 | 01 | 11 | 10 |
|----|----|----|--------|--------|
| 0 | 0 | 1 | Φ | Φ |
| 1 | 0 | 0 | Φ | Φ |

$$J1 = Q0.Q2$$

Q1 Q0

| K1 | 00 | 01 | 11 | 10 |
|----|--------|--------|----|----|
| 0 | Φ | Φ | 0 | 0 |
| 1 | Φ | Φ | 1 | 0 |

$$K1 = Q0.Q2$$

Q1 Q0

| J2 | 00 | 01 | 11 | 10 |
|----|--------|--------|--------|--------|
| 0 | 0 | 0 | 0 | 1 |
| 1 | Φ | Φ | Φ | Φ |

$$J2 = \overline{Q0}.Q1$$

Q1 Q0

| K2 | 00 | 01 | 11 | 10 |
|----|--------|--------|--------|--------|
| 0 | Φ | Φ | Φ | Φ |
| 1 | 1 | 0 | 0 | 0 |

$$K2 = \overline{Q0}.Q1$$

Feel free to use the blank space below if you need to: